

SCHEMATIC LAB 2 PART 1

Power Supply Circuit

